

APPLICATION NOTE

The long range readers are using separate power supply, since the power from the controller is insufficient. In that case, the ground of the reader's power supply and the ground of the controllers power supply **MUST** be connected, as depicted below.

